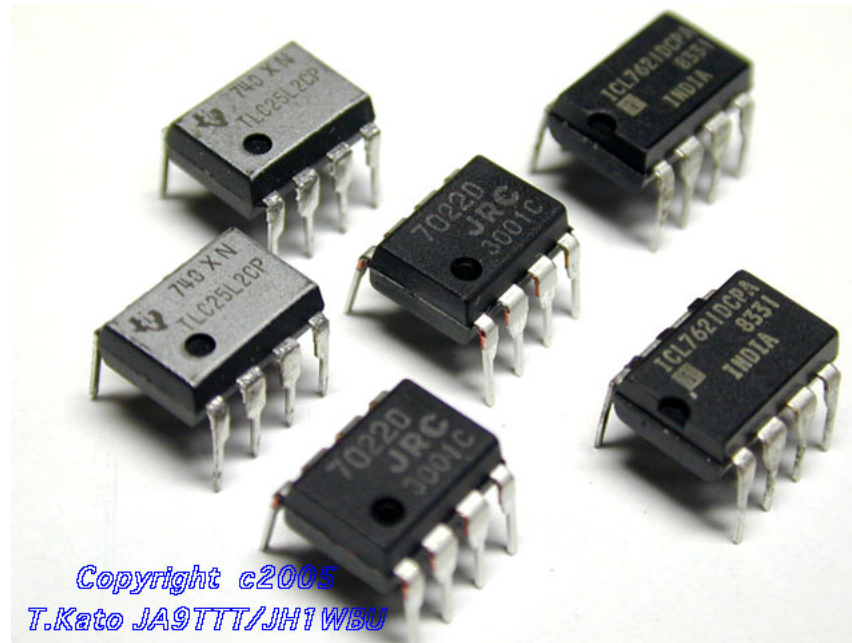


Tom Murphy, UCSD

<http://physics.ucsd.edu/~tmurphy/phys121/phys121.html>



*Copyright c2005  
T.Kato JA9TTT/JH1WBU*



## Operational Amplifiers

Magic Rules

Application Examples
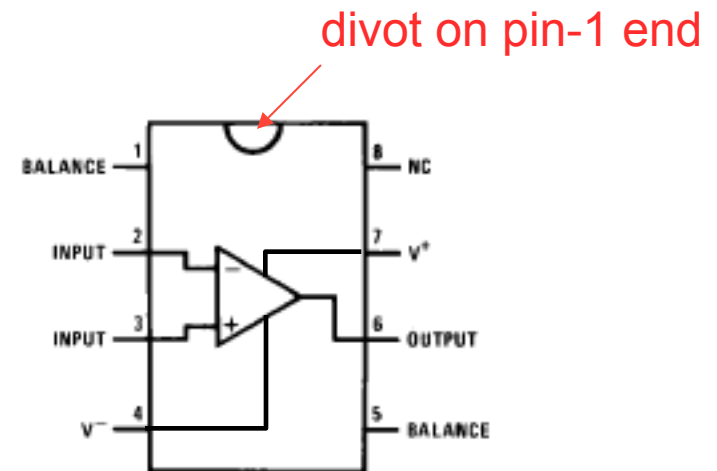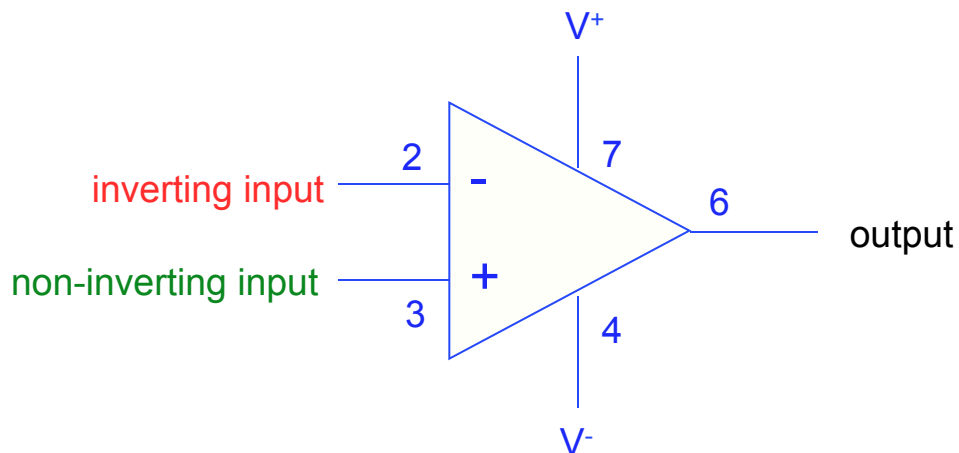
# Op-Amp Introduction


- Op-amps (amplifiers/buffers in general) are drawn as a triangle in a circuit schematic
- There are two inputs
  - inverting and non-inverting
- And one output
- Also power connections (note no explicit ground)



# The ideal op-amp

- Infinite voltage gain
  - a voltage difference at the two inputs is magnified infinitely
  - in truth, something like 200,000
  - means difference between + terminal and - terminal is amplified by 200,000!
- Infinite input impedance
  - no current flows into inputs
  - in truth, about  $10^{12} \Omega$  for FET input op-amps
- Zero output impedance
  - rock-solid independent of load
  - roughly true up to current maximum (usually 5–25 mA)
- Infinitely fast (infinite bandwidth)
  - in truth, limited to few MHz range
  - slew rate limited to 0.5–20 V/ $\mu$ s

# op amp: modello

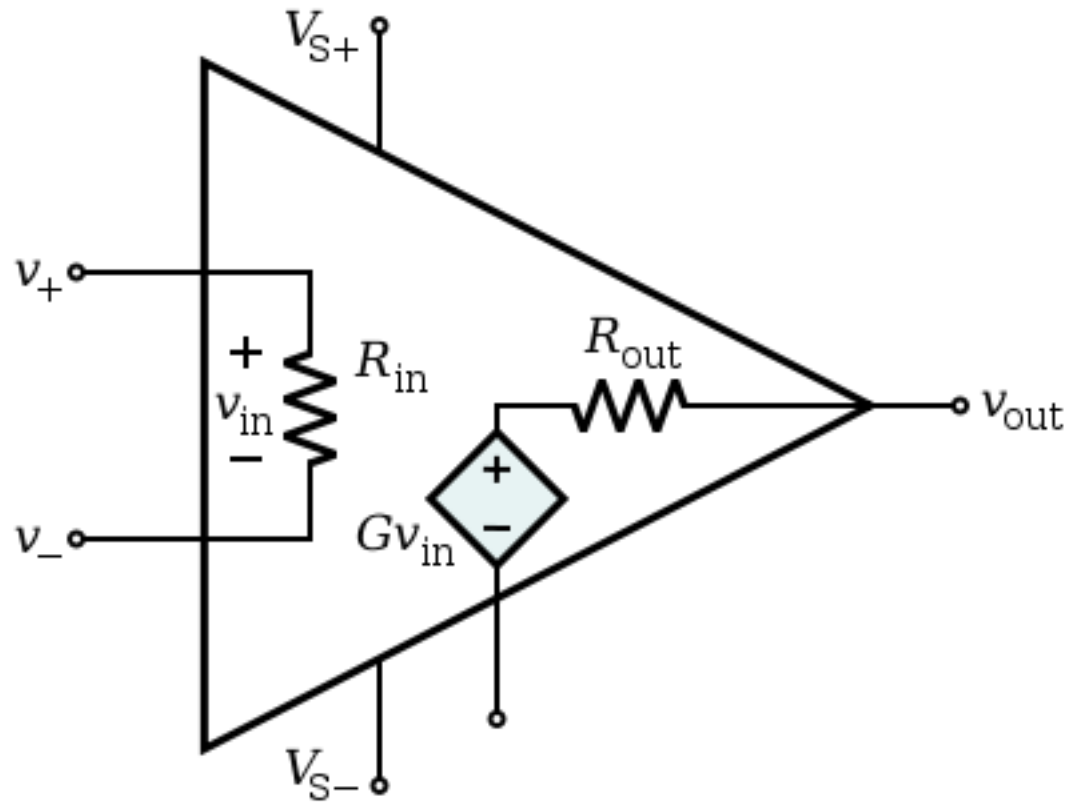


# Op-amp without feedback

- The internal op-amp formula is:

$$V_{\text{out}} = \text{gain} \times (V_+ - V_-)$$

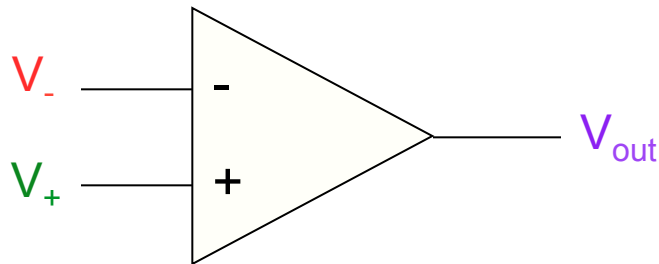
- So if  $V_+$  is greater than  $V_-$ , the output goes positive
- If  $V_-$  is greater than  $V_+$ , the output goes negative



- A **gain** of 200,000 makes this device (as illustrated here) practically useless

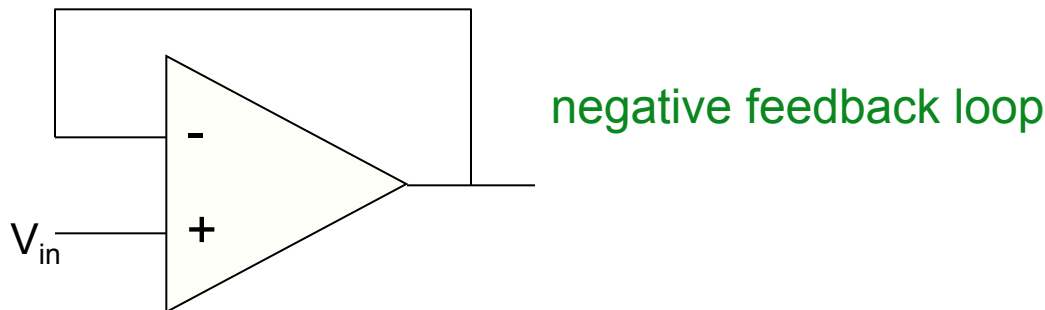
# Infinite Gain in negative feedback

- Infinite gain would be useless except in the self-regulated negative feedback regime
  - negative feedback seems bad, and positive good—but in electronics positive feedback means runaway or oscillation, and negative feedback leads to stability
- Imagine hooking the output to the inverting terminal:
- If the output is less than  $V_{in}$ , it shoots positive
- If the output is greater than  $V_{in}$ , it shoots negative
  - result is that output quickly forces itself to be exactly  $V_{in}$


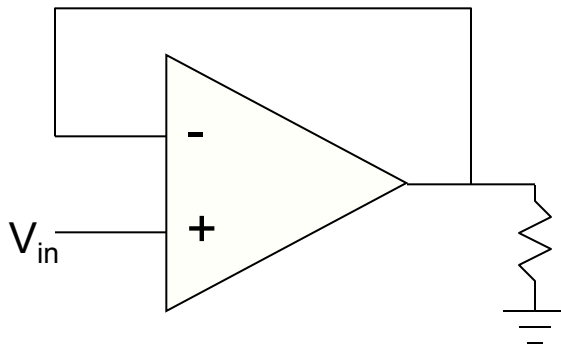
# Even under load


- Even if we load the output (which as pictured wants to drag the output to ground)...
  - the op-amp will do **everything it can** within its current limitations to drive the output until the inverting input reaches  $V_{in}$
  - negative feedback makes it **self-correcting**
  - in this case, the op-amp drives (or pulls, if  $V_{in}$  is negative) a current through the load until the output equals  $V_{in}$
  - so what we have here is a **buffer**: can apply  $V_{in}$  to a load **without burdening** the source of  $V_{in}$  with *any* current!



**Important note:** op-amp output terminal sources/sinks current **at will**: **not like** inputs that have no current flow
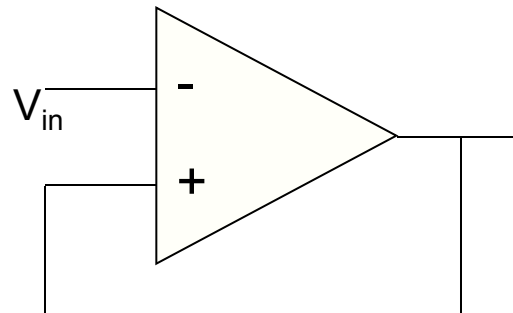
# Positive feedback pathology


- In the configuration below, if the + input is even a smidge higher than  $V_{in}$ , the output goes way positive
- This makes the + terminal even *more* positive than  $V_{in}$ , making the situation worse
- This system will immediately “**rail**” at the supply voltage
  - could rail either direction, depending on initial offset



positive feedback: **BAD**



# feedback

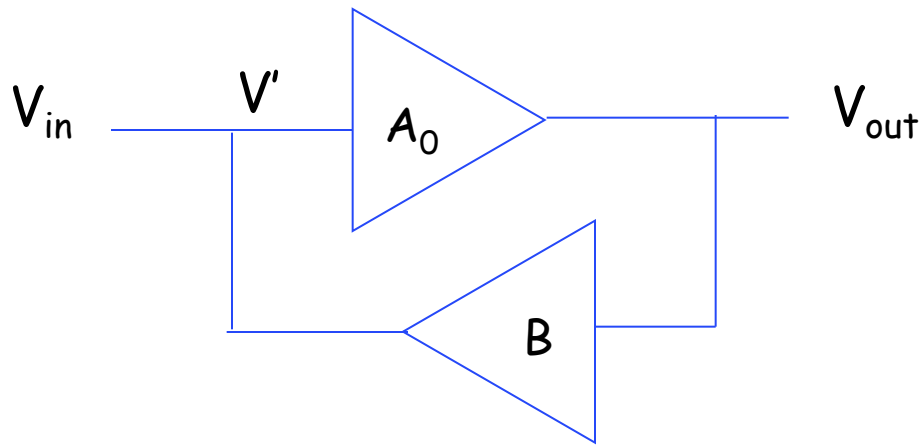

$$A = \frac{V_{out}}{V_{in}}$$

$$V_{out} = A_o V'$$

$$V' = V_{in} + \beta V_{out}$$

$$V_{out} = A_o (V_{in} + \beta V_{out})$$

$$V_{out} (1 - \beta A_o) = A_o V_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{A_o}{(1 - \beta A_o)}$$


$$A = \frac{A_o}{(1 - \beta A_o)}$$

$$A = \frac{A_o}{(1 + \beta A_o)} \sim \frac{1}{\beta}$$


# Op-Amp “Golden Rules”

- When an op-amp is configured in *any* negative-feedback arrangement, it will obey the following two rules:
  - The inputs to the op-amp **draw or source no current** (true whether negative feedback or not)
  - The op-amp output will do **whatever it can** (within its limitations) to make the **voltage difference** between the two inputs **zero**

# Inverting amplifier example

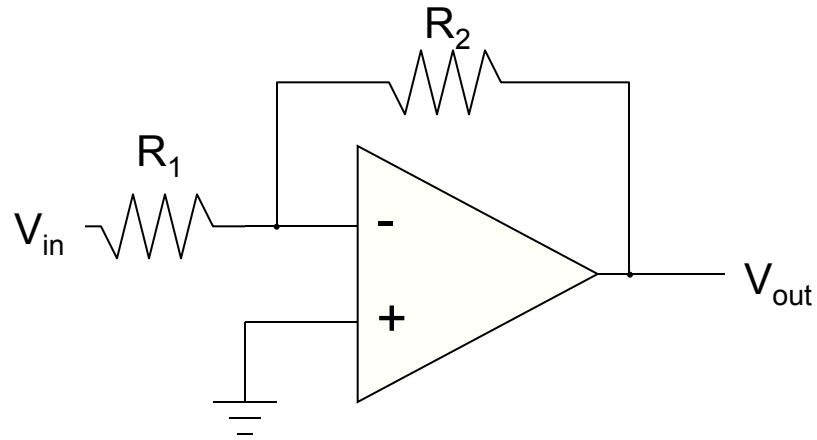


# Inverting amplifier example

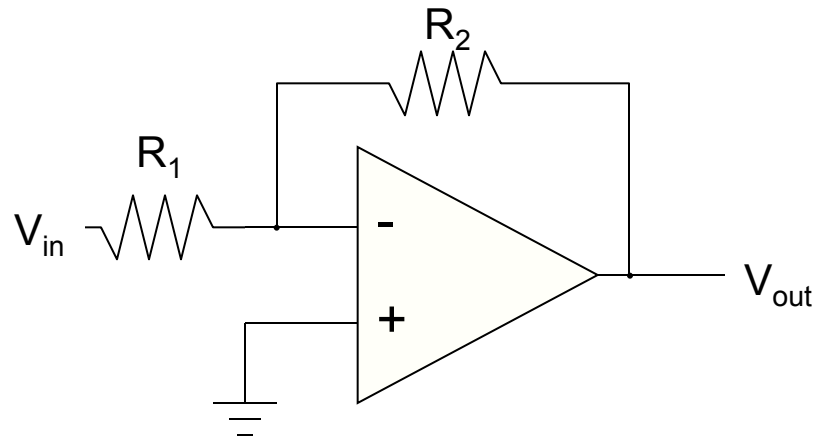


- Applying the rules: - terminal at “virtual ground”
  - so current through  $R_1$  is  $I_f = V_{in}/R_1$
- Current does not flow into op-amp (one of our rules)
  - so the current through  $R_1$  must go through  $R_2$
  - voltage drop across  $R_2$  is then  $I_f R_2 = V_{in} \times (R_2/R_1)$
- So  $V_{out} = 0 - V_{in} \times (R_2/R_1) = -V_{in} \times (R_2/R_1)$
- Thus we amplify  $V_{in}$  by factor  $-R_2/R_1$ 
  - negative sign earns title “inverting” amplifier
- Current is *drawn into* op-amp output terminal


# Non-inverting Amplifier

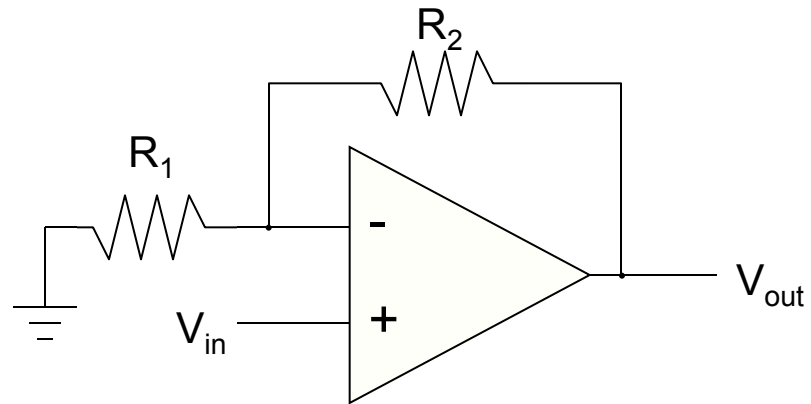

# Non-inverting Amplifier

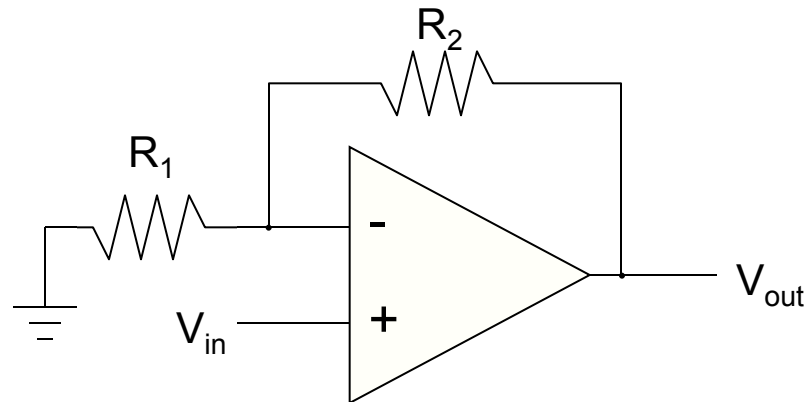


- Now neg. terminal held at  $V_{in}$ 
  - so current through  $R_1$  is  $I_f = V_{in}/R_1$  (to left, into ground)
- This current cannot come from op-amp input
  - so comes through  $R_2$  (delivered from op-amp output)
  - voltage drop across  $R_2$  is  $I_f R_2 = V_{in} \times (R_2/R_1)$
  - so that output is higher than neg. input terminal by  $V_{in} \times (R_2/R_1)$
  - $V_{out} = V_{in} + V_{in} \times (R_2/R_1) = V_{in} \times (1 + R_2/R_1)$
  - thus gain is  $(1 + R_2/R_1)$ , and is positive
- Current is **sourced** from op-amp output in this example

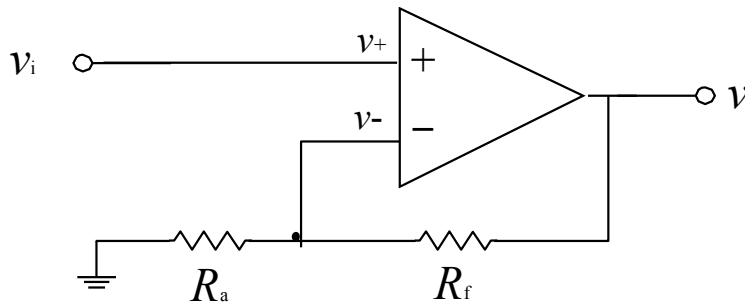


Noninverting amplifier
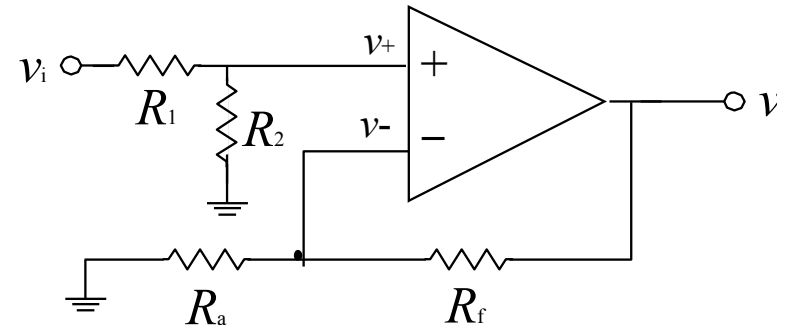
$$v_o = \left(1 + \frac{R_f}{R_a}\right)v_i$$




Noninverting input with voltage divider
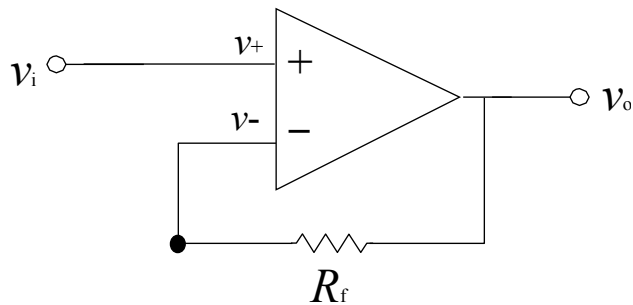
$$v_o = \left(1 + \frac{R_f}{R_a}\right)\left(\frac{R_2}{R_1 + R_2}\right)v_i$$



Voltage follower

$$v_o = v_i$$


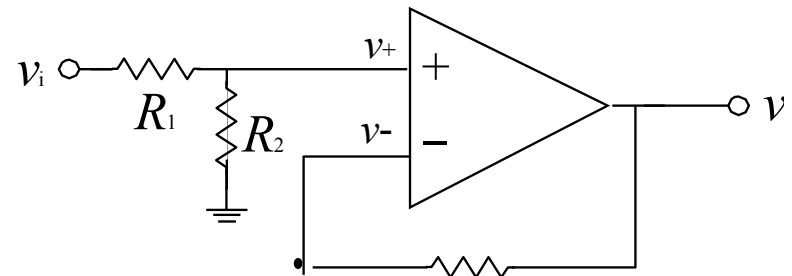


Less than unity gain

$$v_o = \frac{R_2}{R_1 + R_2} v_i$$


# Ideal Vs Practical Op-Amp

	Ideal	Practical
Open Loop gain $A$	$\infty$	$10^5$
Bandwidth $BW$	$\infty$	10-100Hz
Input Impedance $Z_{in}$	$\infty$	$>1M\Omega$
Output Impedance $Z_{out}$	$0 \Omega$	10-100 $\Omega$
Output Voltage $V_{out}$	Depends only on $V_d = (V_+ - V_-)$ Differential mode signal	Depends slightly on average input $V_c = (V_+ + V_-)/2$ Common-Mode signal
CMRR	$\infty$	10-100dB

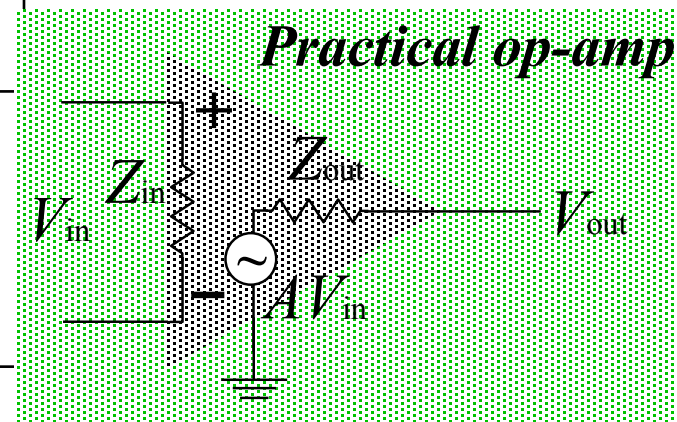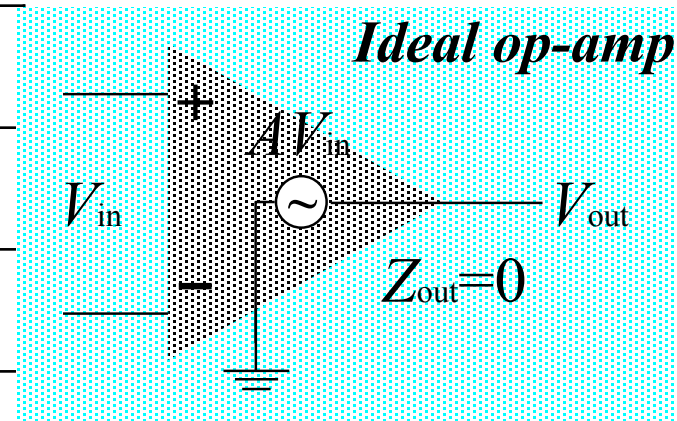




# Summing Amplifier

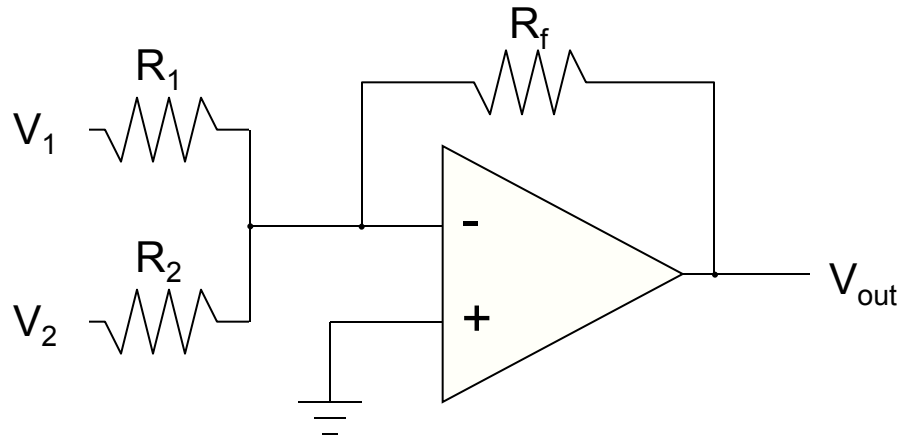


- Much like the inverting amplifier, but with two input voltages
  - inverting input still held at virtual ground
  - $I_1$  and  $I_2$  are added together to run through  $R_f$
  - so we get the (inverted) sum:  $V_{out} = -R_f \times (V_1/R_1 + V_2/R_2)$ 
    - if  $R_2 = R_1$ , we get a sum proportional to  $(V_1 + V_2)$
- Can have any number of summing inputs
  - we'll make our D/A converter this way

# Differencing Amplifier

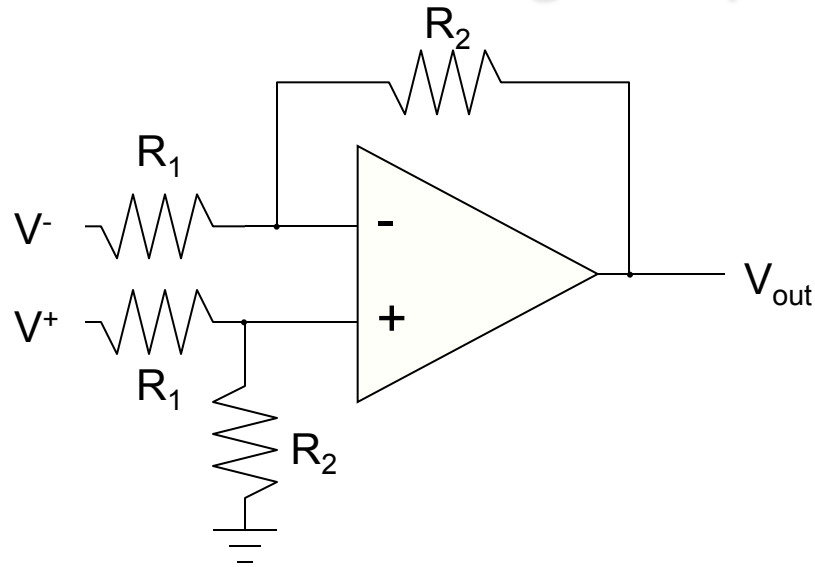


- The non-inverting input is a simple voltage divider:

# Differencing Amplifier

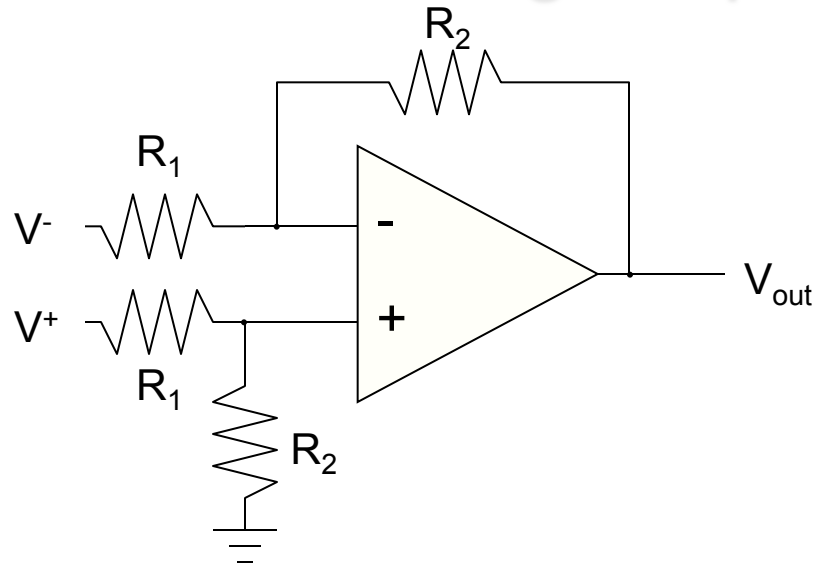


- The non-inverting input is a simple voltage divider:
  - $V_{\text{node}} = V^+ R_2 / (R_1 + R_2)$

# Differencing Amplifier

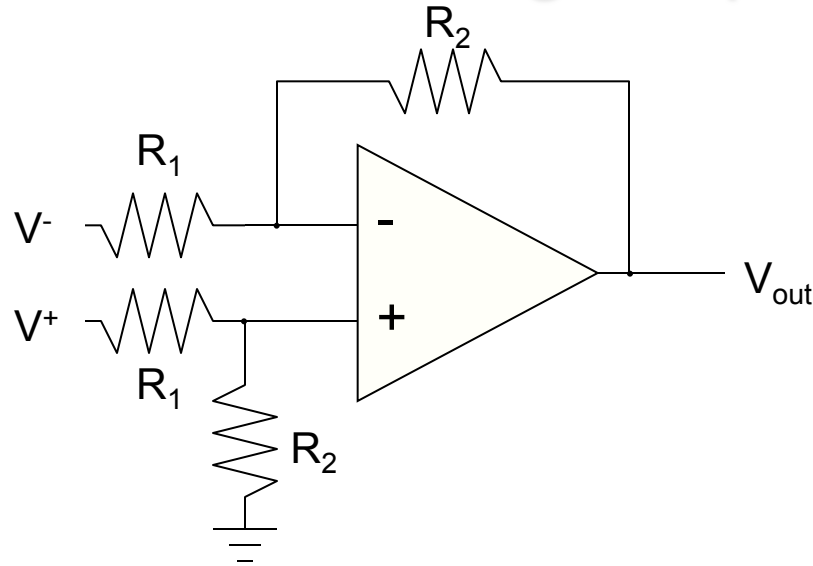


- The non-inverting input is a simple voltage divider:
  - $V_{node} = V^+ R_2 / (R_1 + R_2)$
- So  $I_f = (V^- - V_{node}) / R_1$

# Differencing Amplifier

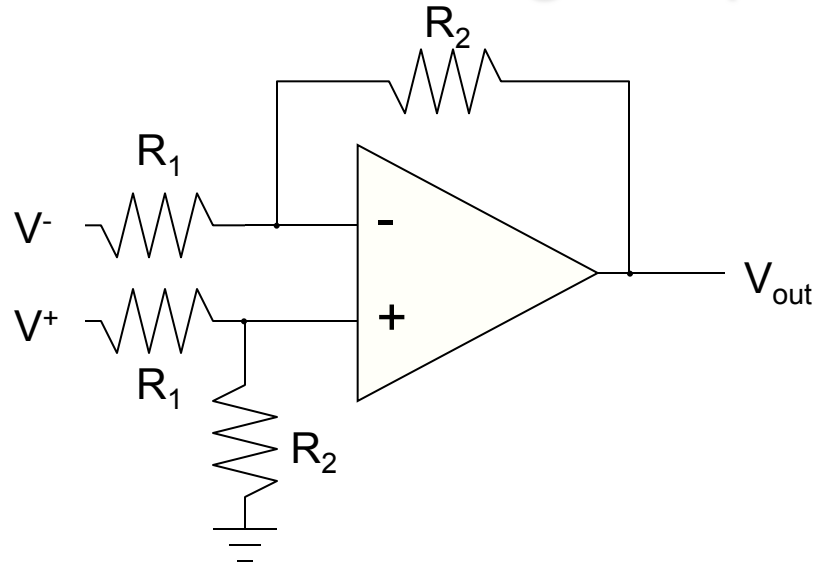


- The non-inverting input is a simple voltage divider:
  - $V_{node} = V^+ R_2 / (R_1 + R_2)$
- So  $I_f = (V^- - V_{node}) / R_1$ 
  - $V_{out} = V_{node} - I_f R_2 = V^+ (1 + R_2 / R_1) (R_2 / (R_1 + R_2)) - V^- (R_2 / R_1)$

# Differencing Amplifier

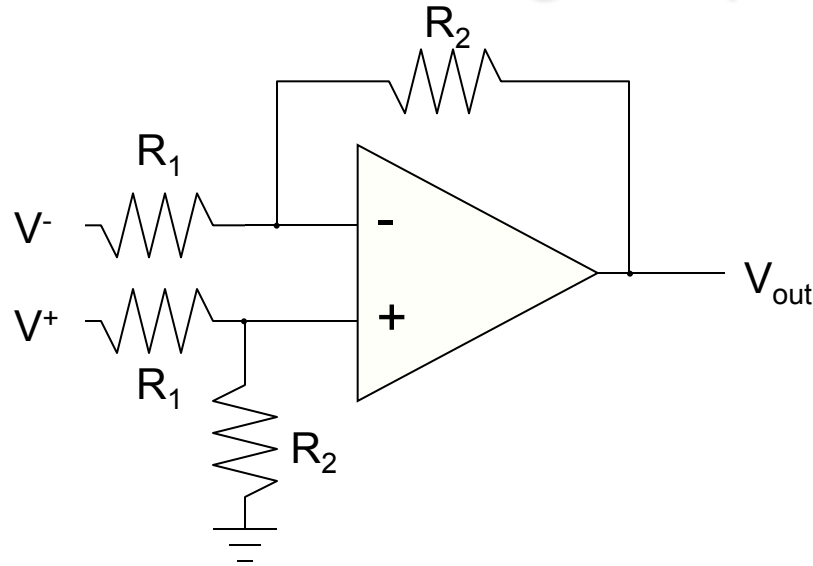

- The non-inverting input is a simple voltage divider:
  - $V_{\text{node}} = V^+ R_2 / (R_1 + R_2)$
- So  $I_f = (V^- - V_{\text{node}}) / R_1$ 
  - $V_{\text{out}} = V_{\text{node}} - I_f R_2 = V^+ (1 + R_2 / R_1) (R_2 / (R_1 + R_2)) - V^- (R_2 / R_1)$
  - so  $V_{\text{out}} = (R_2 / R_1) (V^+ - V^-)$

# Differentiator (high-pass)

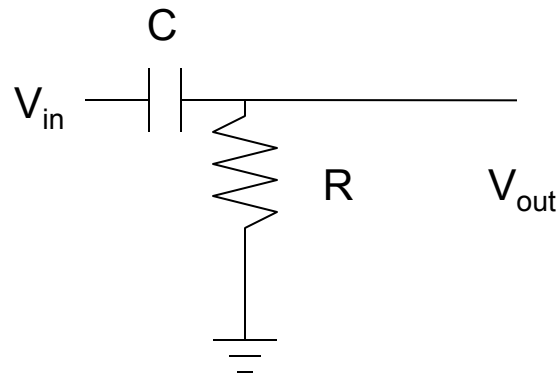

$$Q = CV$$


$$I = \frac{dQ}{dt} = C \frac{dV}{dt}$$

$$I = C \frac{d}{dt} (V_{in} - V_{out}) = \frac{V_{out}}{R}$$

$$\frac{dV_{out}}{dt} \ll \frac{dV_{in}}{dt} \quad C \frac{dV_{in}}{dt} = \frac{V_{out}}{R}$$

$$V_{out} = RC \frac{dV_{in}}{dt}$$

# Differentiator (high-pass)

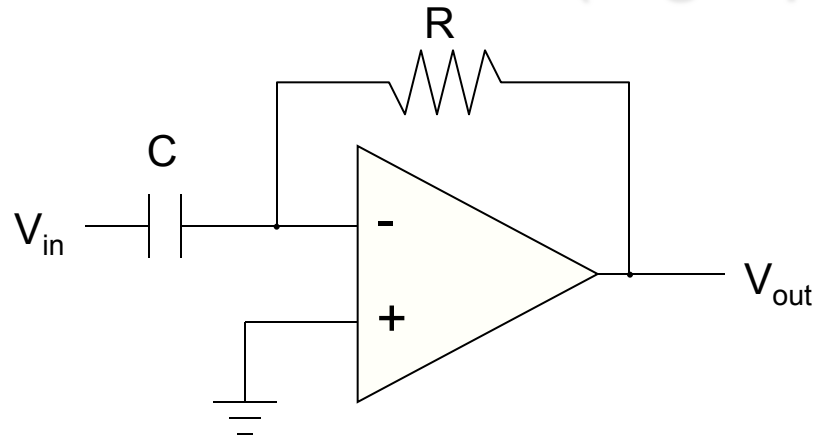

- For a capacitor

$$Q = CV$$


$$I = \frac{dQ}{dt} = C \frac{dV}{dt}$$

$$V_{out} = -I_{cap}R = -RC \frac{dV}{dt}$$

- So we have a differentiator, or high-pass filter



# Low-pass filter (integrator)

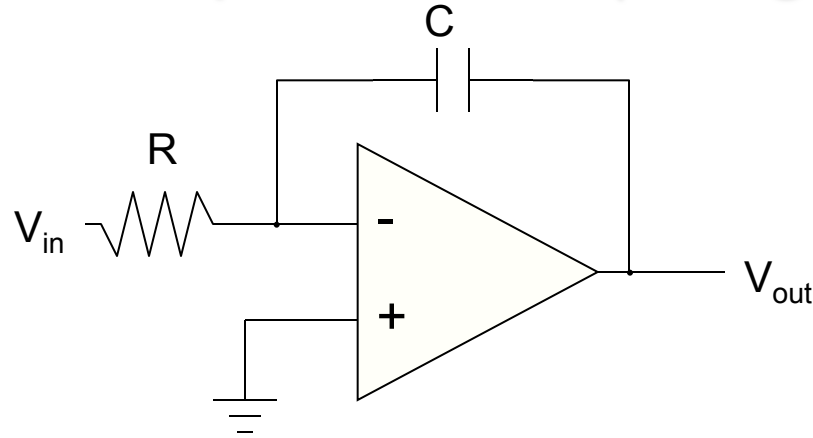

$$Q = CV$$

$$I = \frac{dQ}{dt} = C \frac{dV}{dt}$$

- $I_f = V_{in}/R$ , so  $C \cdot dV_{cap}/dt = V_{in}/R$


– and since left side of capacitor is at virtual ground:

$$-\frac{dV_{out}}{dt} = \frac{V_{in}}{RC}$$

$$V_{out} = -\frac{1}{RC} \int V_{in} dt$$


– and therefore we have an integrator (low pass)

# esempio: 741

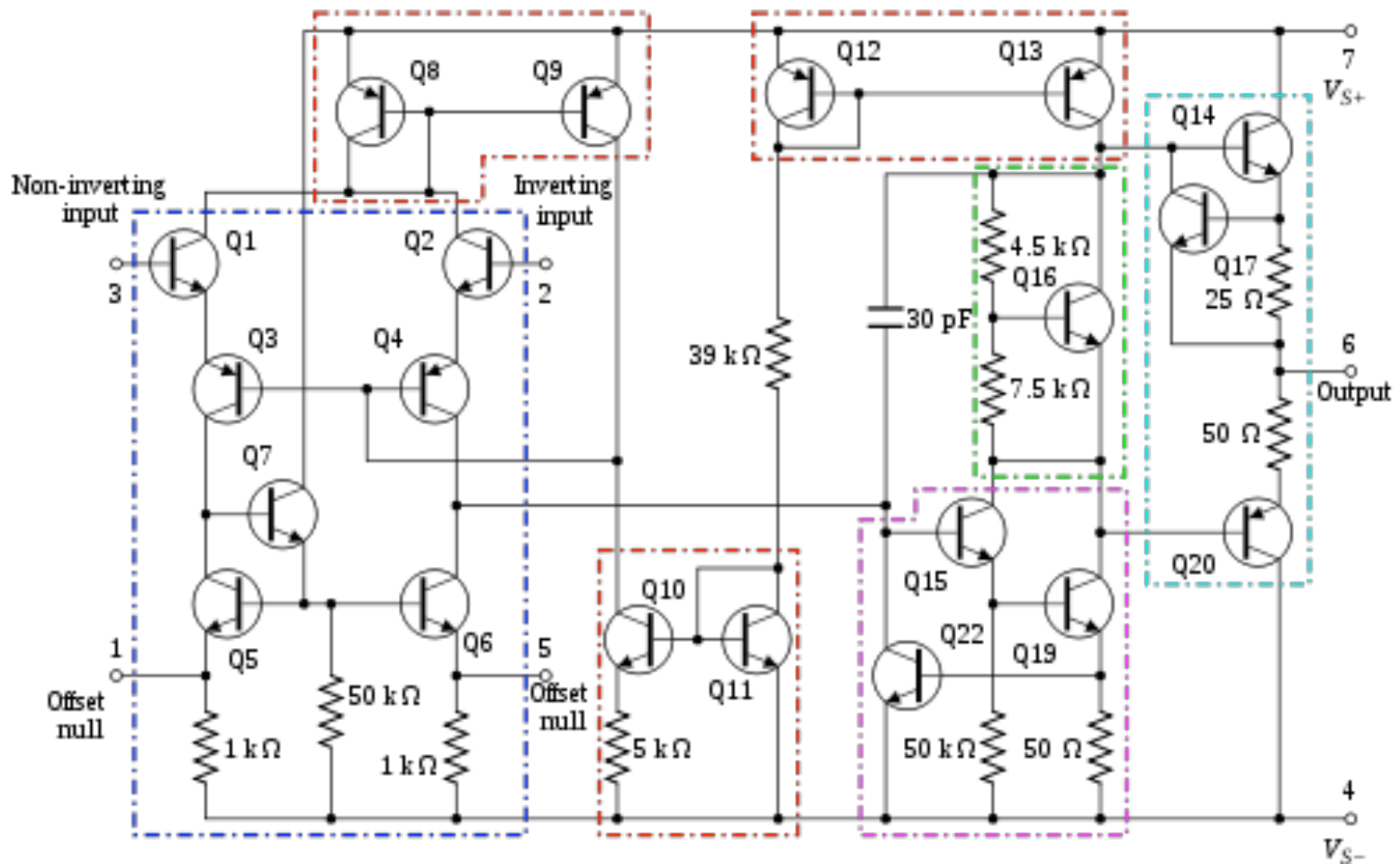
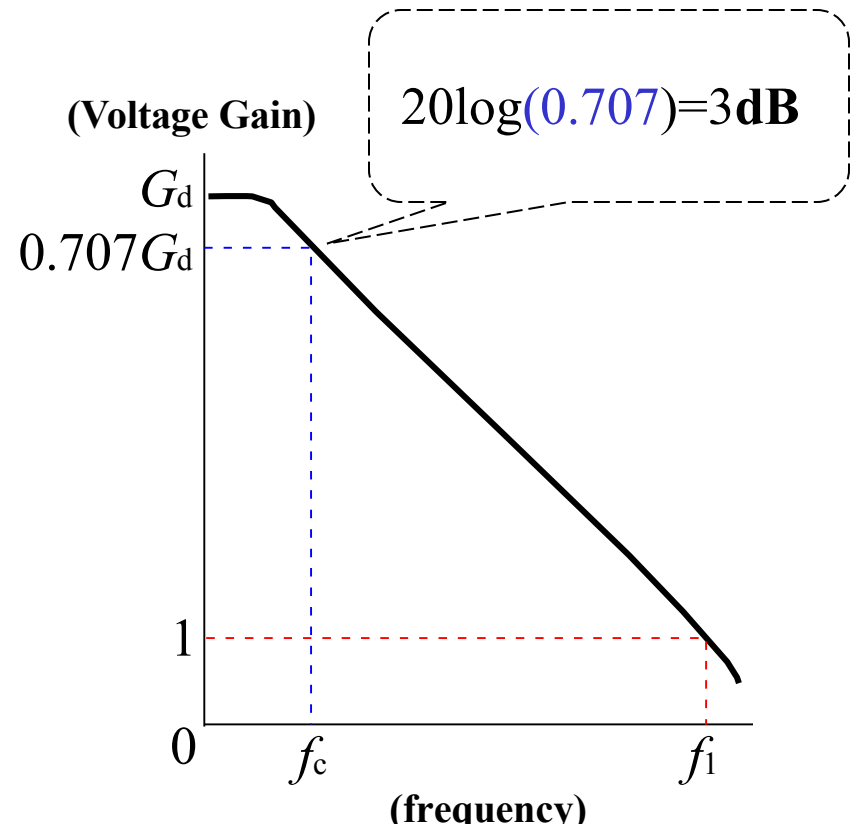
# Frequency-Gain Relation

- Ideally, signals are amplified from DC to the highest AC frequency
- Practically, bandwidth is limited
- 741 family op-amp have an limit bandwidth of few KHz.
- Unity Gain frequency  $f_1$ : the gain at unity
- Cutoff frequency  $f_c$ : the gain drop by 3dB from dc gain  $G_d$



$$\text{GB Product : } f_1 = G_d f_c$$

# GB Product

Example: Determine the cutoff frequency of an op-amp having a unit gain frequency  $f_1 = 10 \text{ MHz}$  and voltage differential gain  $G_d = 20 \text{ V/mV}$

Sol:

Since  $f_1 = 10 \text{ MHz}$


By using GB production equation


$$f_1 = G_d f_c$$

$$f_c = f_1 / G_d = 10 \text{ MHz} / 20 \text{ V/mV}$$

$$= 10 \times 10^6 / 20 \times 10^3$$

$$= 500 \text{ Hz}$$

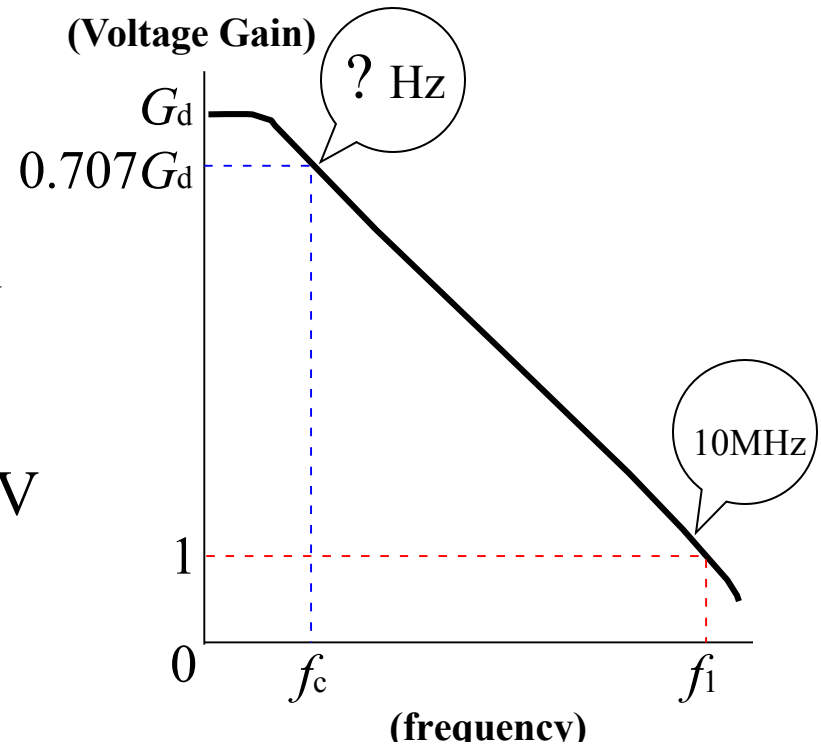

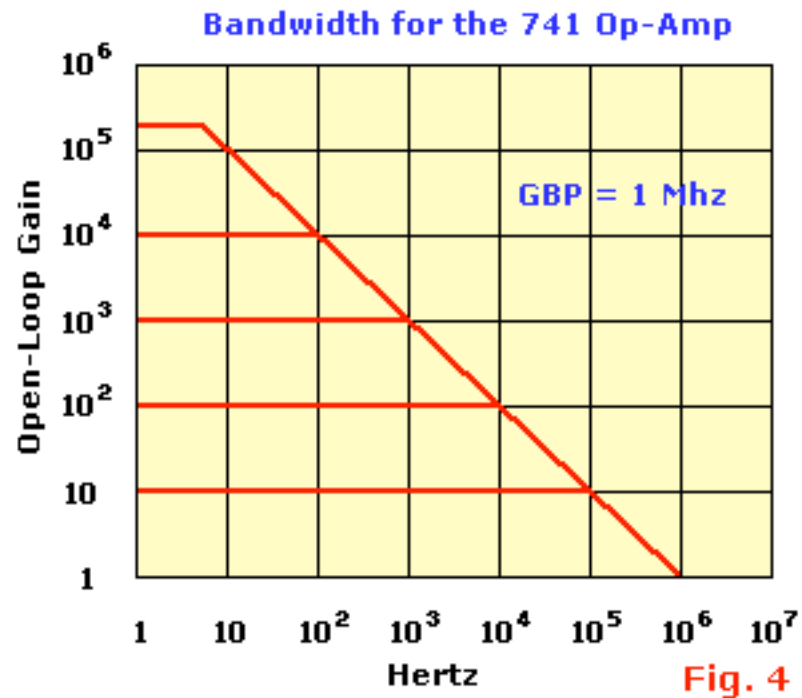

Gain-Bandwidth product:  $GBP = A_o BW$