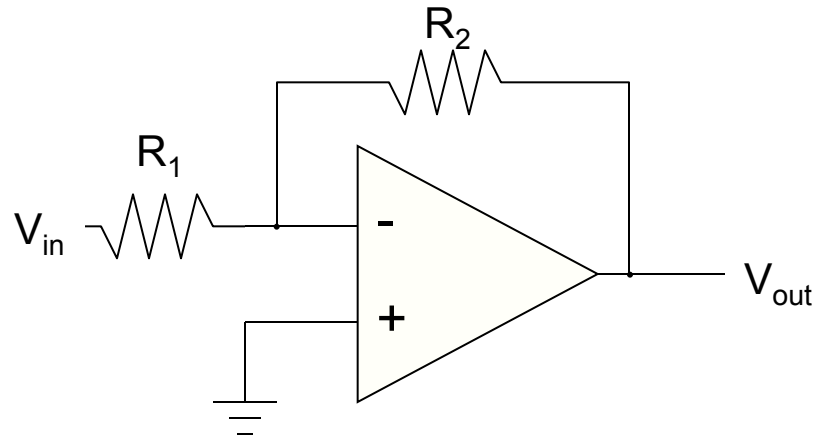


Esercizio n° 2


- Si realizzino i seguenti montaggi basati sull'amplificatore operazione 741 e se ne descriva il funzionamento:
 - amplificatore
 - amplificatore invertente
 - integratore o derivatore
- Si caratterizzino in modo quantitativo gli amplificatori al variare della frequenza del segnale in ingresso
- Si verifichi la banda passante di uno dei due amplificatori al variare del guadagno

Inverting amplifier example




- Applying the rules: - terminal at “virtual ground”
 - so current through R_1 is $I_f = V_{in}/R_1$
- Current does not flow into op-amp (one of our rules)
 - so the current through R_1 must go through R_2
 - voltage drop across R_2 is then $I_f R_2 = V_{in} \times (R_2/R_1)$
- So $V_{out} = 0 - V_{in} \times (R_2/R_1) = -V_{in} \times (R_2/R_1)$
- Thus we amplify V_{in} by factor $-R_2/R_1$
 - negative sign earns title “inverting” amplifier
- Current is *drawn into* op-amp output terminal

Non-inverting Amplifier

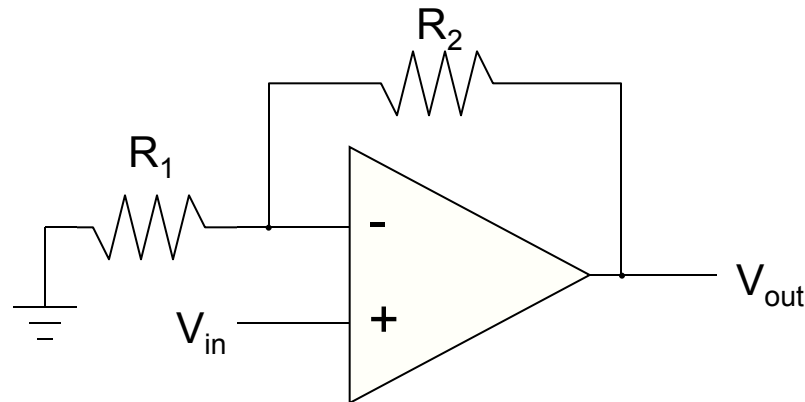


- Now neg. terminal held at V_{in}
 - so current through R_1 is $I_f = V_{in}/R_1$ (to left, into ground)
- This current cannot come from op-amp input
 - so comes through R_2 (delivered from op-amp output)
 - voltage drop across R_2 is $I_f R_2 = V_{in} \times (R_2/R_1)$
 - so that output is higher than neg. input terminal by $V_{in} \times (R_2/R_1)$
 - $V_{out} = V_{in} + V_{in} \times (R_2/R_1) = V_{in} \times (1 + R_2/R_1)$
 - thus gain is $(1 + R_2/R_1)$, and is positive
- Current is **sourced** from op-amp output in this example

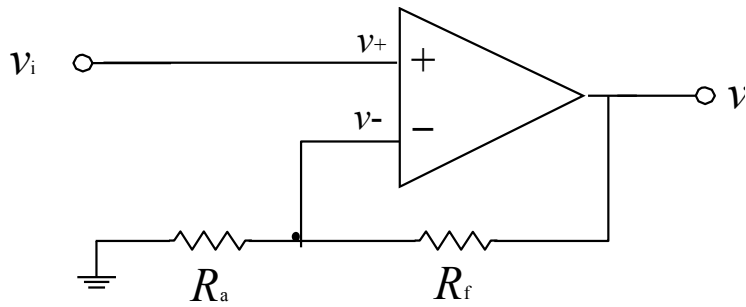


Noninverting amplifier
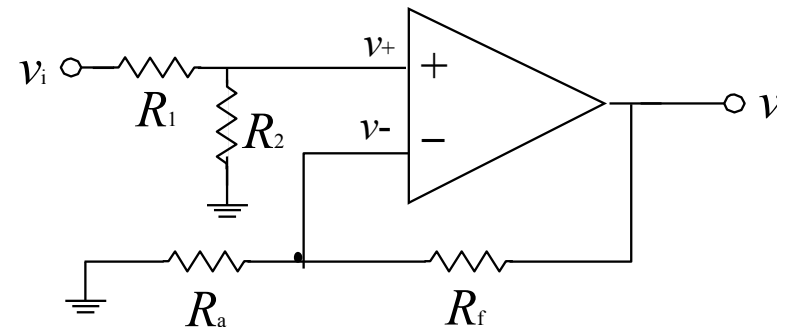
$$v_o = \left(1 + \frac{R_f}{R_a}\right)v_i$$




Noninverting input with voltage divider
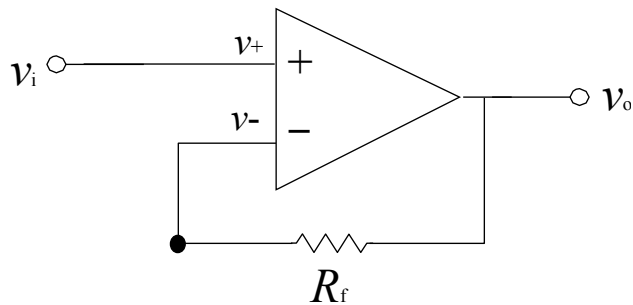
$$v_o = \left(1 + \frac{R_f}{R_a}\right)\left(\frac{R_2}{R_1 + R_2}\right)v_i$$



Voltage follower


$$v_o = v_i$$

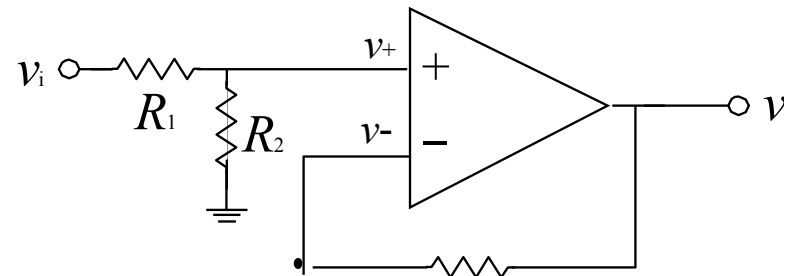

Less than unity gain


$$v_o = \frac{R_2}{R_1 + R_2} v_i$$

Summing Amplifier

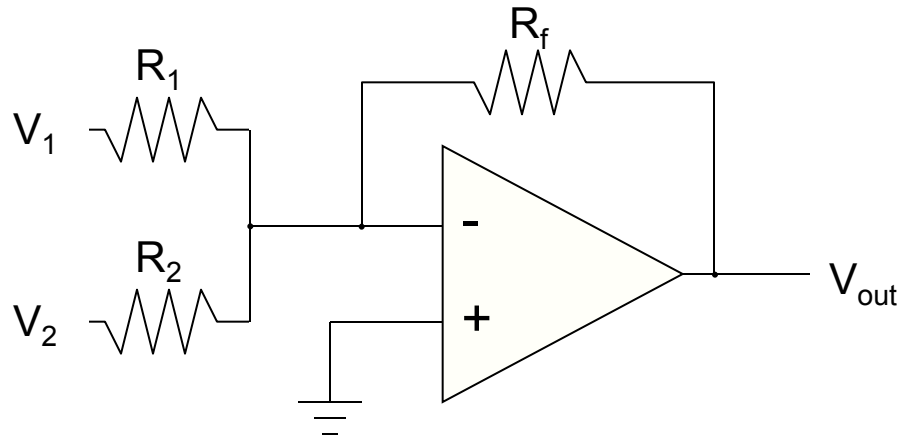


- Much like the inverting amplifier, but with two input voltages
 - inverting input still held at virtual ground
 - I_1 and I_2 are added together to run through R_f
 - so we get the (inverted) sum: $V_{out} = -R_f \times (V_1/R_1 + V_2/R_2)$
 - if $R_2 = R_1$, we get a sum proportional to $(V_1 + V_2)$
- Can have any number of summing inputs
 - we'll make our D/A converter this way

Differencing Amplifier

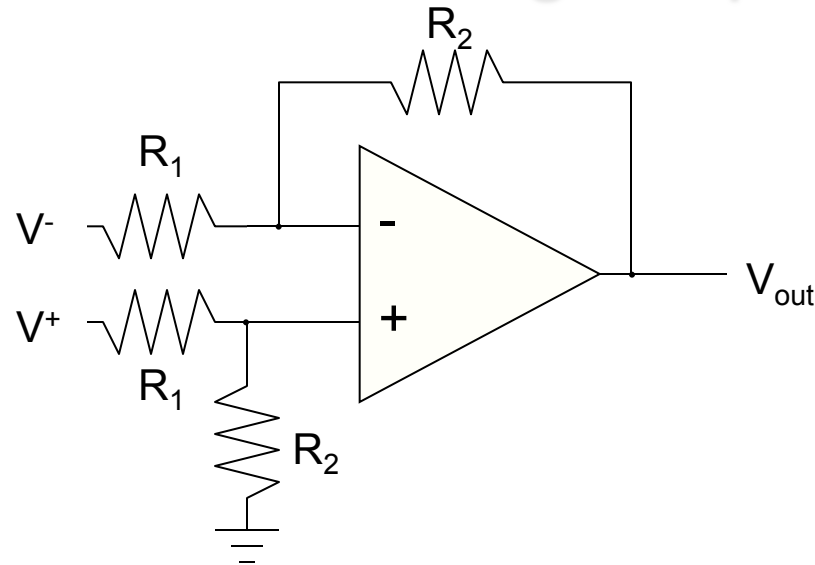

- The non-inverting input is a simple voltage divider:
 - $V_{\text{node}} = V^+ R_2 / (R_1 + R_2)$
- So $I_f = (V^- - V_{\text{node}}) / R_1$
 - $V_{\text{out}} = V_{\text{node}} - I_f R_2 = V^+ (1 + R_2 / R_1) (R_2 / (R_1 + R_2)) - V^- (R_2 / R_1)$
 - so $V_{\text{out}} = (R_2 / R_1) (V^+ - V^-)$

Differentiator (high-pass)

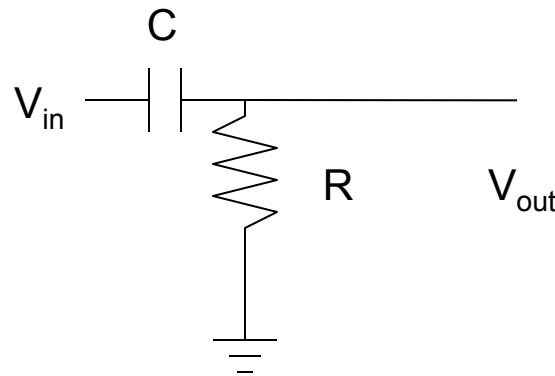

$$Q = CV$$


$$I = \frac{dQ}{dt} = C \frac{dV}{dt}$$

$$I = C \frac{d}{dt} (V_{in} - V_{out}) = \frac{V_{out}}{R}$$

$$\frac{dV_{out}}{dt} \ll \frac{dV_{in}}{dt} \quad C \frac{dV_{in}}{dt} = \frac{V_{out}}{R}$$

$$V_{out} = RC \frac{dV_{in}}{dt}$$

Differentiator (high-pass)

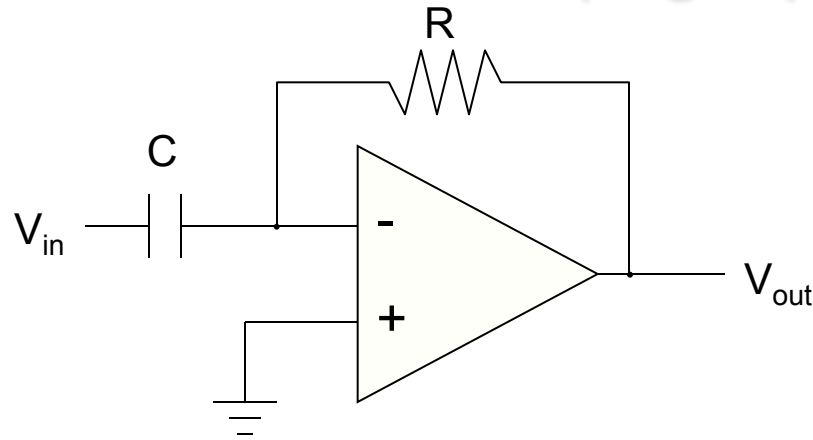

- For a capacitor


$$Q = CV$$

$$I = \frac{dQ}{dt} = C \frac{dV}{dt}$$

$$V_{out} = -I_{cap}R = -RC \frac{dV}{dt}$$

- So we have a differentiator, or high-pass filter

Low-pass filter (integrator)

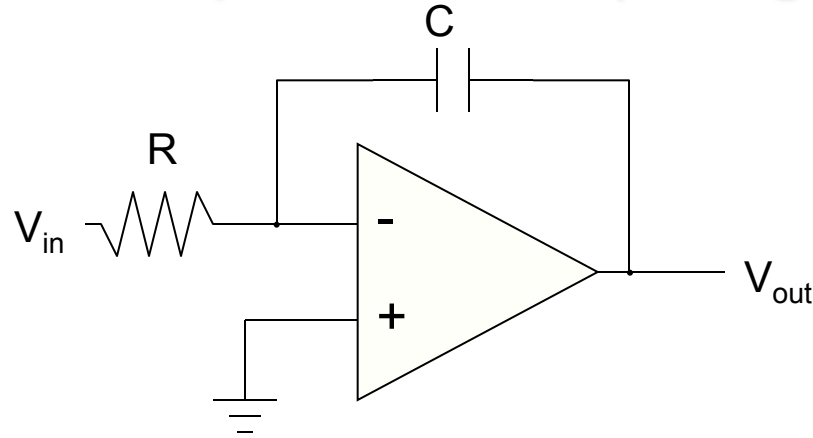

$$Q = CV$$

$$I = \frac{dQ}{dt} = C \frac{dV}{dt}$$

- $I_f = V_{in}/R$, so $C \cdot dV_{cap}/dt = V_{in}/R$

– and since left side of capacitor is at virtual ground:

$$-\frac{dV_{out}}{dt} = \frac{V_{in}}{RC}$$

$$V_{out} = -\frac{1}{RC} \int V_{in} dt$$

– and therefore we have an integrator (low pass)